

1. Ohmov zakon

Taj Šobot

January 15, 2026

1 1. zaporedna in vzporedna vezava

Fitan graf za enosmerni tok:

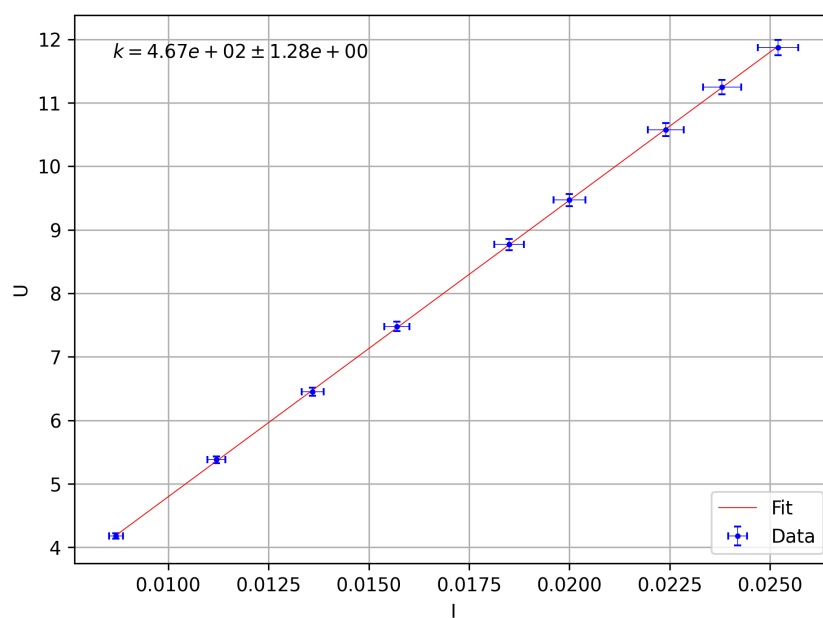


Figure 1: Graf1

$$R = (467 \pm 1)\Omega$$

Fitan graf za izmenični tok:

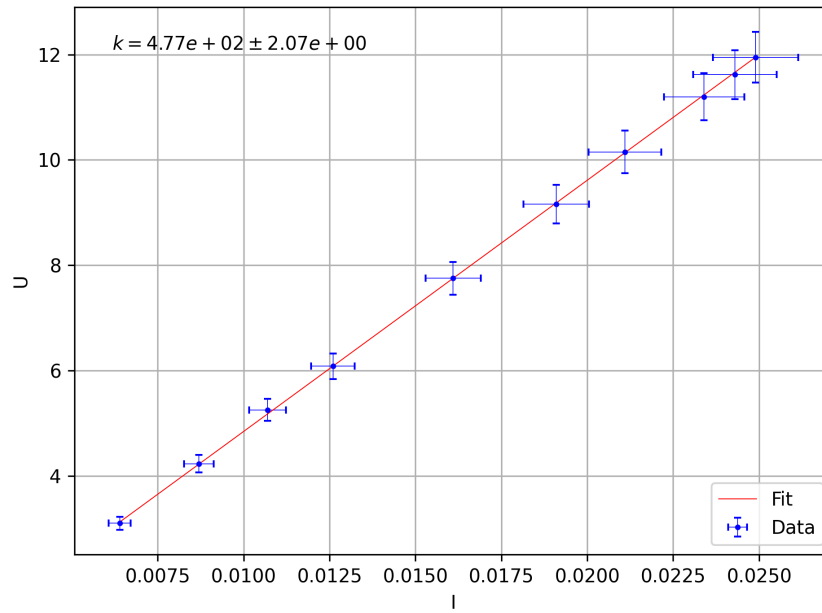


Figure 2: Graf2

$$R = (477 \pm 2)\Omega$$

2 2. velik upor